Marking Scheme

OBAFEMI AWOLOWO UNIVERSITY, ILE-IFE, NIGERIA DEPARTMENT OF PHYSICS AND ENGINEERING PHYSICS *PHY 203: ELECTRICAL CIRCUITS & ELECTRONICS*

2022/2023 Mid-semester Test, Date: 29th Jan., 2024 Time Allowed: 3/4 hour Department:

- - 1. Which of the following statements is true about the Kirchoff's laws?
 - A. Kirchoff's law is equivalent to Ohm's law
 - B. The conservation of energy and conservation of charge when applied to electrical circuits are known as Kirchoff's law
 - C. Conservation of energy in an electrical circuit means that the algebraic sum of the voltage drops, $\sum_i V_i = Constant$ around a closed circuit loop (imaginary loop)
 - D. Conservation of charge zero algebraic sum of the currents $\sum_k I_k = Constant$ Ik flowing into a point (total charge in, equals total charge out)
 - E. None of the above
 - 2. In Figure 1 below, the voltage across the terminals AB in the voltage divider is

A.
$$V_{out} = \frac{R_1}{R_2} V_{in}$$

B. $V_{out} = \frac{R_2}{R_1} V_{in}$
D. $V_{out} = \frac{R_1}{R_1 + R_2} V_{in}$
E. None of the above

3. In Figure 2 below, the current, I_3 , which flows through the resistor, R_3 , is

A.
$$I_3 = \frac{R_2}{R_1 + R_2 + R_3} I$$
 B. $I_3 = \frac{R_1 R_2}{R_1 + R_2 + R_3} I$ C. $I_3 = \frac{R_1 R_2 R_3}{R_1 + R_2 + R_3}$
 $D I_3 = \frac{R_1 R_2}{R_1 R_2 + R_2 R_3 + R_3 R_1} I$ E. None of the above

- 4. A combination of elements and Kirchoff's laws can give an equivalent circuit. There are two possibilities. These are:
 - A. Ohm's equivalent circuit; Superposition circuit
 - B. Thevenin equivalent circuit; Norton equivalent circuit
 - C. Superposition circuit; Transformer circuit
 - D. Ohm's equivalent circuit; Transformer equivalent circuit
 - E. None of the above
- 5. On the basis of their purpose, a Transformer can be either
 - A Step up transformer; or A Step down transformer
 - B. A core type transformer; or A shell type transformer
 - C. A Copper winding transformer; or An Iron winding transformer
 - D. A Power transformer; Line transformer
 - E. None of the above

Questions 6 and 7 are based on Figure 3 above,

- 6. Given that V = 75 volts, R₁ = R₂ = R₃ = 5 Ω. Calculate the current which flows through the R₃ resistor. A. 20 A B. 15 A C. 5 A D. 10 A E. None of the above
 7. The voltage, V₂ is,
- A. 50 V B. 25 V C. 75 V D. 30 V E. None of the above
- Which of the following Statements about the transformer is true?
 A. A transformer is an ideal device which has no losses.





I



1

- 1.1
- B. A transformer is another form of a transistor.
- C. A transformer has 50% losses.

D. A transformer has two losses: Core losses and Copper losses

E. None of the above

9. Which of the following Statements is false?

 \mathcal{A} . The capacitance C between two appropriate surfaces is defined by $VC = \frac{Q}{R}$

- B. Since Q and E can be stored a capacitor can be used as a (non-ideal) source of I and V
- C. Faraday's law applied to an inductor states that a changing current induces a back EMF that opposes the change.

D. Unlike the capacitor which behaves like an open-circuit in DC circuits, an inductor behaves like a short circuit in DC circuits.

E. None of the above

10. In Figure 4, the current which flows in the circuit is

A. $I(t) = V(0)e^{-t/_{RC}}$ B. $I(t) = I(0)e^{-t/_{RC}}$ C. $I(t) = V(0)e^{-t/_{RC}}$ D. $I(0) = V(0)e^{-t/_{RC}}$ E. None of the above



- 11. Metals or good conductors conduct electricity by virtue of free electrons
- 13. At what temperature does a semiconductor behave as a perfect insulator Absolute zero
- 14. A meter that can measure resistance, D.C and A.C currents or voltages effectively is .Multimeter
- 15. Two major views by which material can be classified are lonization potential and Energy bands
- 16. An impurity atom that produces p-type conductivity by creation of hole is Acceptor Impurity.

17. The use of D.C voltage to eliminate potential barrier and allow flow of current in the circuit of a p-n junction device is forward Biasing.

- 18. A simple electronic component that converts A.C current or voltage to D.C component is Rectifier
- 19. The property of a material that determines whether it is semiconductor or not is . Resistivity

20. In practical use, when currents are hindered at p-n junction of an electronic device due to established high potential barrier, a very small current that still flows in the circuit is <u>Reverse</u> Saturation current 21. A transistor operates with a collector current of 100mA and an emitter current of 102mA. Determine the value of base current. <u>2mA</u>

- 22. What are the Three basic circuit configurations used for transistor <u>Emitter</u> <u>Collector</u> base
- 23. A bipolar transistor has a common-emitter current gain of 125. If the transistor operates with a collector current of 50mA, determine the value of base current. <u>400 MA</u>
- 24. A field effect transistor operates with a drain current of 100mA and a gate source bias of -1V. The device has a gfs (common-source dynamic forward transfer conductance) value of 0.25. If the bias voltage decreases to -1.1V, determine (a) the change in drain current, and (b) the new value of drain current. <u>-25mA</u> <u>75mA</u>
- 25. In normal operation an n-p-n transistor connected in common-base configuration has
- A. the emitter at a lower potential than the base
- B. the collector at a lower potential than the base
- C. the base at a lower potential than the emitter
- D. the collector at a lower potential than the emitter
- E. None of the above

2